

# Logic Gate to Truth Table Worksheet

Logic Circuit	Truth Table
	
	
	
	