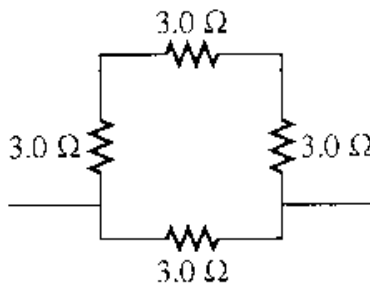


# Equivalent Resistance Worksheet

Name: \_\_\_\_\_


1. Three resistors with values of  $3.0 \Omega$ ,  $6.0 \Omega$ , and  $12 \Omega$  are connected in series. What is the equivalent resistance of this combination?
2. Three resistors with values of  $4.0 \Omega$ ,  $6.0 \Omega$ , and  $12.0 \Omega$  are connected in parallel. What is their equivalent resistance?
3. Two resistors with values of  $6.0 \Omega$  and  $12 \Omega$  are connected in parallel. This combination is connected in series with a  $4.0 \Omega$  resistor. What is the overall resistance of this combination?
4. Three resistors with values of  $18 \Omega$ ,  $26 \Omega$ ,  $9 \Omega$ , respectively, are connected in series. What is their equivalent resistance?
5. Four resistors with values of  $15 \Omega$ ,  $20 \Omega$ ,  $30 \Omega$ ,  $60 \Omega$ , respectively, are connected in parallel. What is the overall resistance of this combination?
6. Two resistors with values of  $6.0 \Omega$  and  $12 \Omega$  are connected in parallel. This combination is connected in series with a  $2.0 \Omega$  resistor and a  $24 \text{ V}$  battery. What is the current in the  $2.0 \Omega$  resistor?




7. What is the equivalent resistance for the resistors in the figure above?

# Equivalent Resistance Worksheet


Name: \_\_\_\_\_

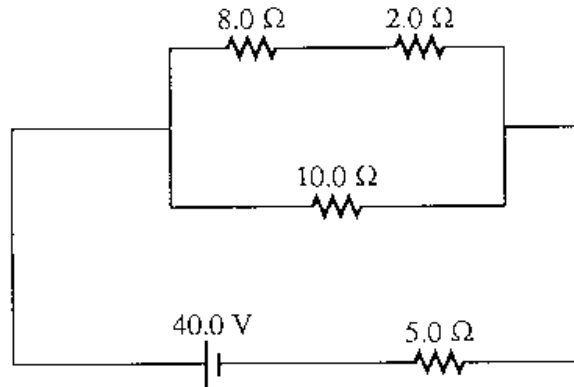

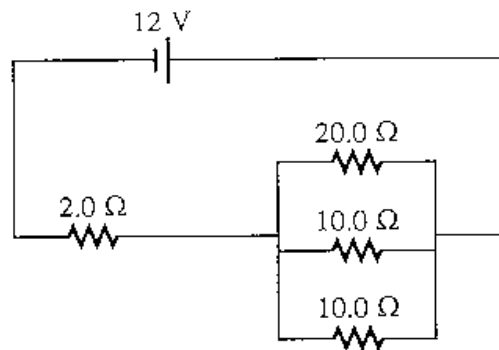8. For the circuit shown above find the following
- What is the equivalent resistance for the resistors in the figure above?
  - What is the total current in the circuit above?



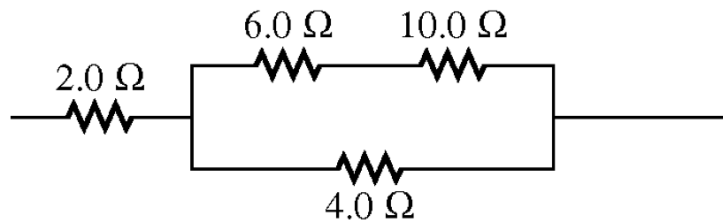9. For the circuit shown above find the following
- What is the equivalent resistance for the resistors in the figure above?
  - What is the total current in the circuit above?



10. For the circuit shown above find the following
- What is the equivalent resistance for the resistors in the figure above?
  - What would the current through the 2 Ω resistor in the figure above if 120V is applied?