

Karnaugh Maps Review

Using the following diagram:

- Write the Boolean expression for the output 'Y'
- Create the truth table for the circuit
- Simplify the Boolean expression using a Karnaugh map
- Draw the simplified logic diagram

