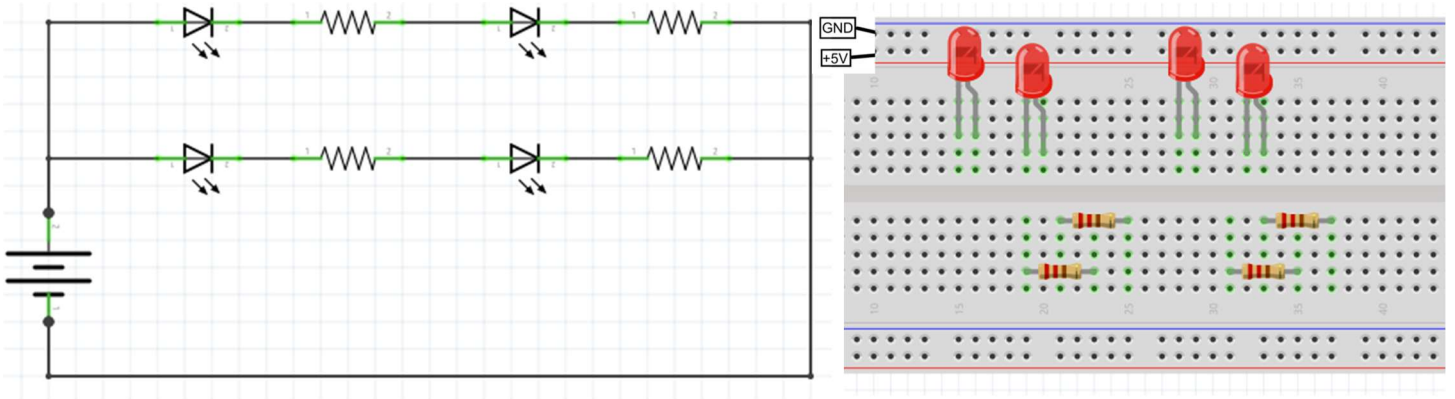


### Breadboarding Practice Test

- Using the schematic and available parts on the breadboard, complete the "wiring" by drawing lines as wires.

NOTE: Make all wires clearly visible and distinct



- Draw a simple circuit diagram to represent what is wired in this example breadboard.

